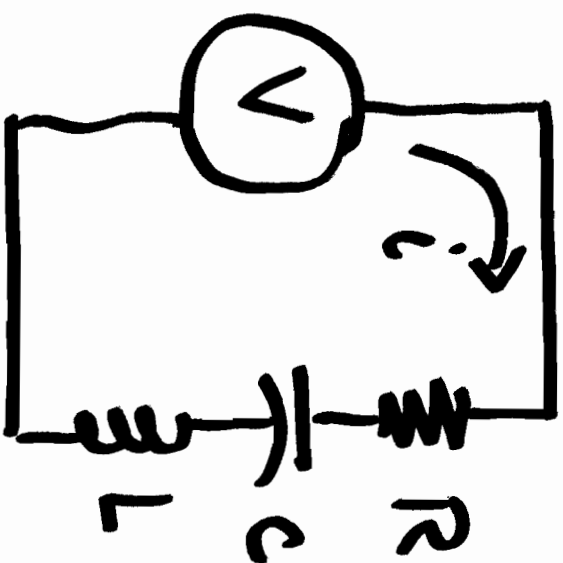


Application of Complex Variables to Analyze Electrical

Systems



Restrict ourselves to

harmonic inputs:

$$v(t) = V_m \cos \omega t = V_m \cos 2\pi f t$$

We seek the steady state

current i .

$$v_R = Ri, \quad v_C = \frac{1}{C} \int i dt, \quad v_L = L \frac{di}{dt}$$

$$v(t) = Ri + \frac{1}{C} \int i dt + L \frac{di}{dt}$$

We can use complex variables to solve for $i(t)$;

$$v(t) \rightarrow \hat{V} e^{j\omega t}, \quad \hat{V} = V + jQ, \quad i(t) = \hat{I} e^{j\omega t}$$

$$\hat{V} = R \hat{I} + \frac{1}{j\omega C} \hat{I} + L j\omega \hat{I}$$

solve for \hat{I} ;

$$\hat{I} = \frac{1}{R + \frac{1}{j\omega C} + j\omega L} \hat{V}$$

$$\text{Given } V, R, C, L, \omega \Rightarrow |I(t)| = |\hat{I}| \cos(\omega t + \arg \hat{I})$$

Like the mechanical system, we can define an impedance for an electrical circuit:

In electrical impedance for a circuit is


$$\hat{Z}_e = \frac{\hat{V}}{\hat{I}} \Rightarrow \hat{V} = \hat{Z}_e \hat{I}$$

For an SSSA RLC circuit; the electrical impedance

is:

$$\hat{Z}_e = R + \frac{1}{j\omega C} + j\omega L$$

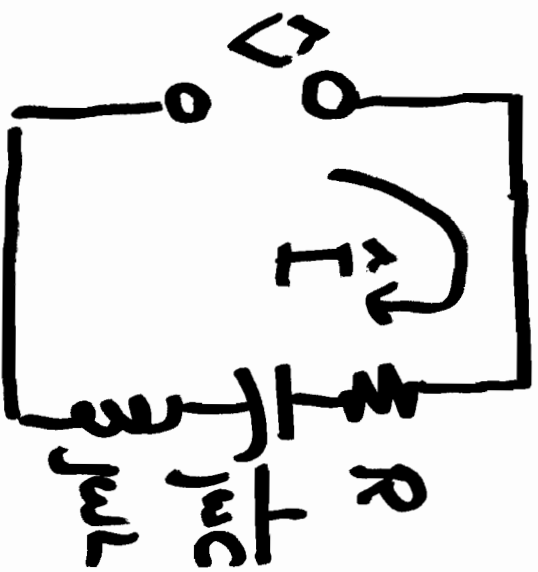Using electrical impedances to solve circuit problems



Resistor $V_R = Ri$; $\hat{V}_R = R\hat{I}$

Capacitor $V_C = \frac{1}{C} \int i dt$; $\hat{V}_C = \frac{1}{j\omega C} \hat{I}$



Inductor $V_L = L \frac{di}{dt}$; $\hat{V}_L = j\omega L \hat{I}$

Using "DC" analysis $\hat{Z}_C = R + \frac{1}{j\omega C} + j\omega L$

$$\hat{V} = (R + \frac{1}{j\omega C} + j\omega L) \hat{I}$$



Examples:

$$V(t) = V \cos \omega t$$

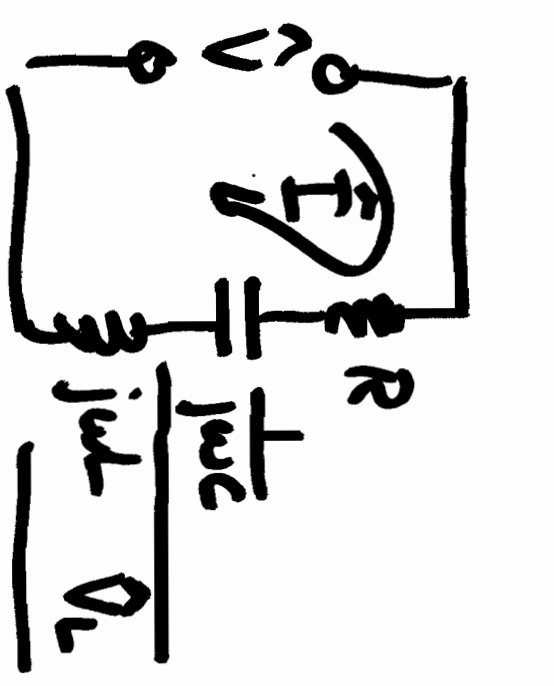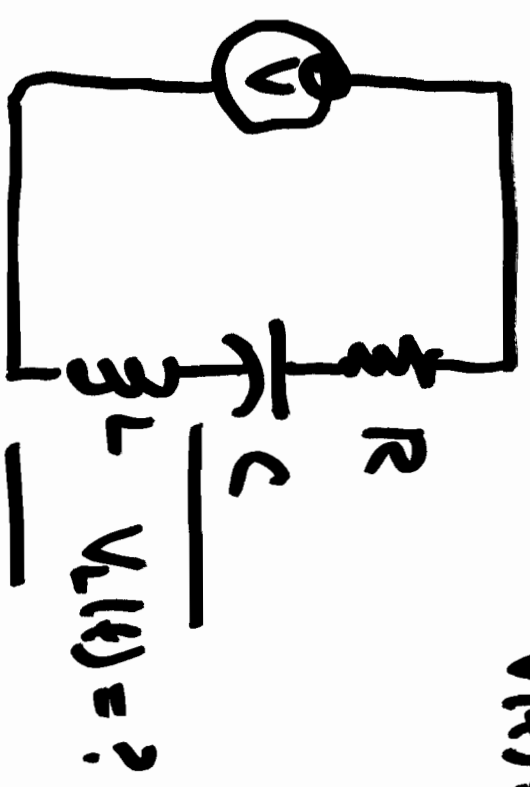

$$\hat{V}_L = \frac{j\omega L}{R + j\omega L + \frac{1}{j\omega C}} \hat{V}$$

$$V_L(t) = |\hat{V}_L| \cos(\omega t + \alpha) \hat{V}_L$$

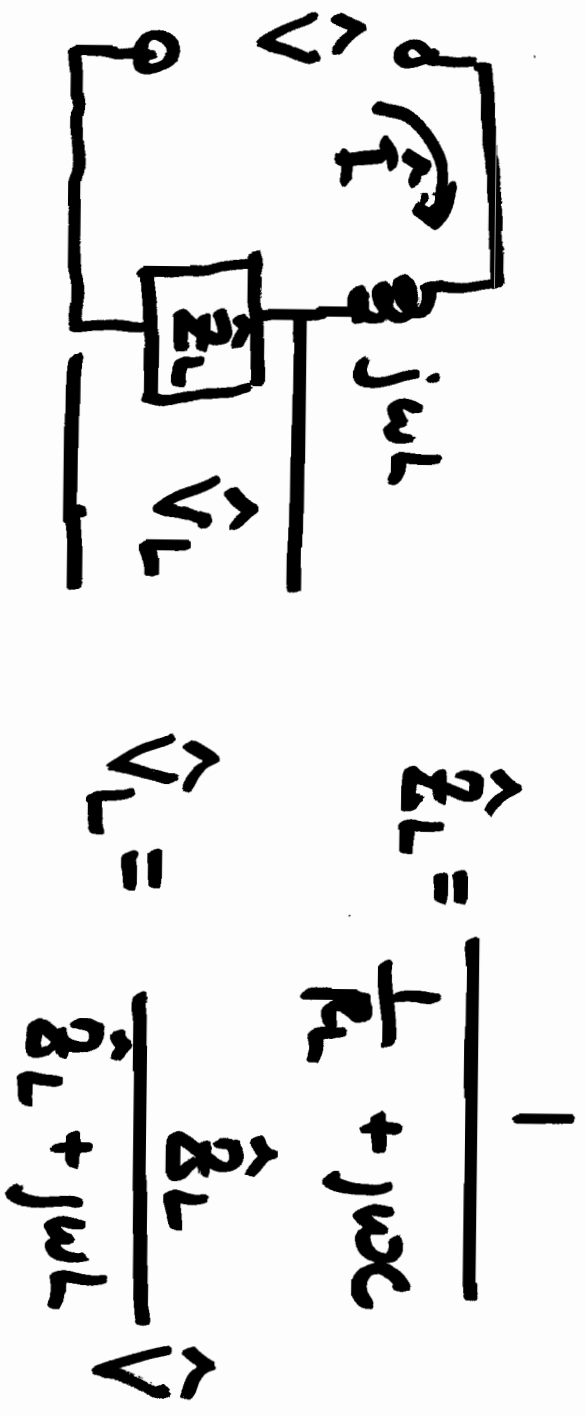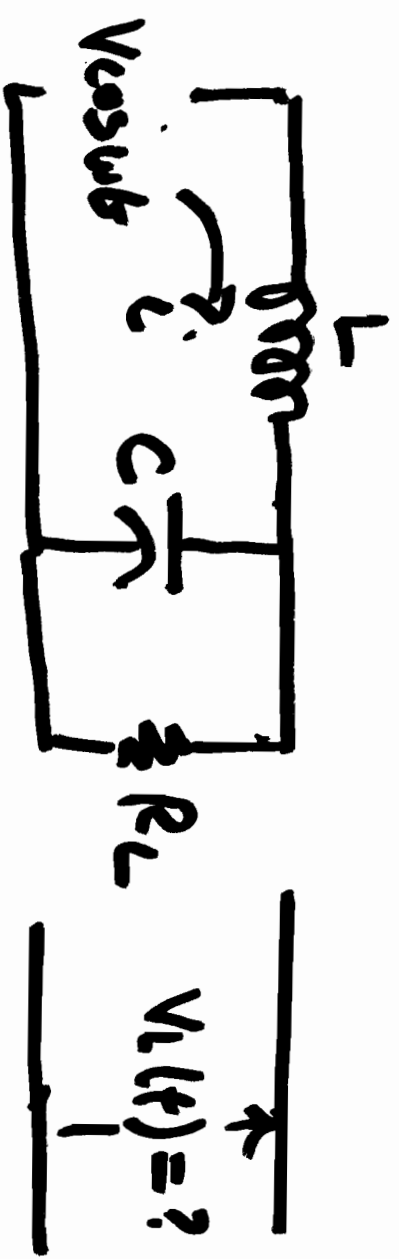

$$\hat{Z}_L = \frac{1}{R_L + j\omega C}$$

$$\hat{V}_L = \frac{\hat{Z}_L}{\hat{Z}_L + j\omega L} \hat{V}$$

$$\hat{V} = (j\omega L + \hat{Z}_L) \hat{I} \Rightarrow \hat{I} = \frac{1}{j\omega L + \hat{Z}_L} \hat{V}$$

$$i(t) = |\hat{I}| \cos(\omega t + \phi_{ij} \hat{I}).$$

Analogy Between Electrical and Mechanical Systems

Mechanical System
(mass-spring-damper)

Electrical System
(series-RLC)

$$F_{\text{result}} = s \int u dt + R_{\text{nu}} + m \dot{u}$$

$$V_{\text{result}} = \frac{1}{C} \int i dt + R_i + L \frac{di}{dt}$$



These systems are analogous because they

share the same differential equation

In the case $F(s) \leftrightarrow V(s)$, $i(s) \leftrightarrow u(s)$


$m \leftrightarrow L$, $R \leftrightarrow R_m$, $1/s \leftrightarrow C$

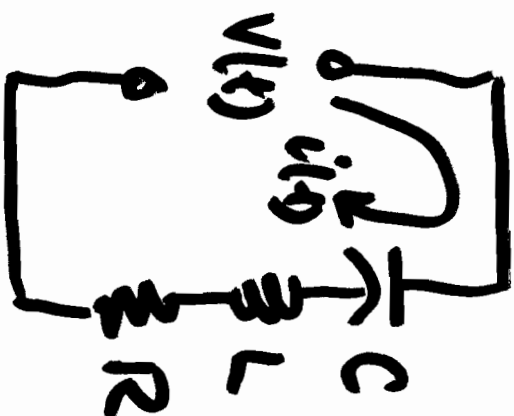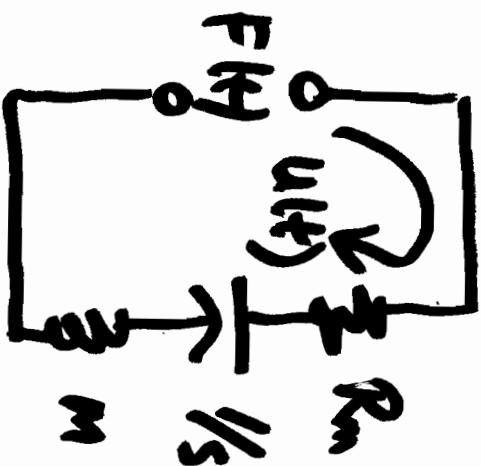We can draw equivalent circuit diagrams...



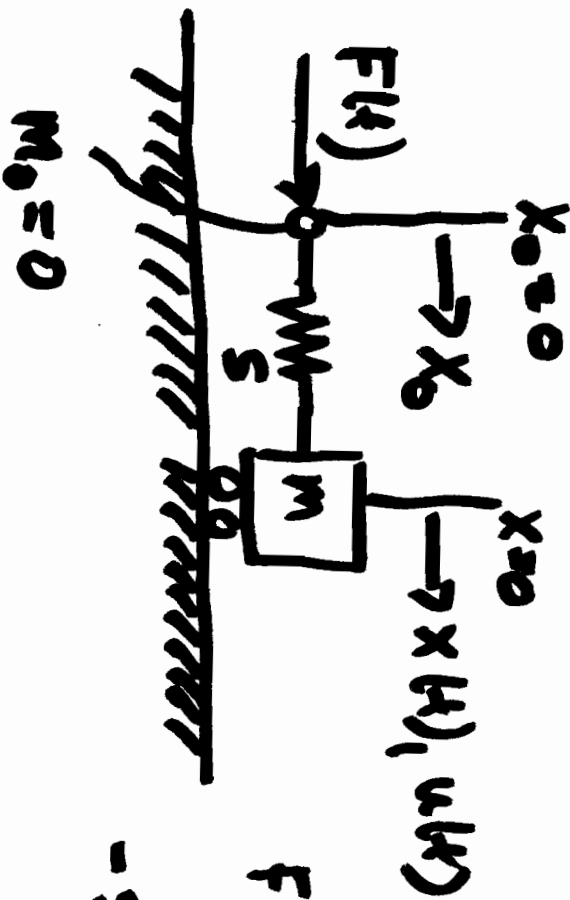Problems in text, given a mechanical system, and asked to find a circuit analog.

Newborn's laws for the following mechanical system...



$$F(t) - S(x_0 - x) = m \ddot{x}$$

$$-S(x - x_0) = m \ddot{x}$$